NEC 304

STLD

Lecture 34

Datapath Analysis

Rajeev Pandey Department Of ECE rajeevvce2007@gmail.com

Overview

° Datapaths must deal with input and output data values

- Implement with tri-state buffers
- ° Necessary to control external interfaces
 - Perform repetitive operations
- ° Some datapaths require decision making
 - Control outputs implemented in ROM
- ° Moving towards software
 - Control implemented as a series of instructions
- $^\circ$ Understanding the data and control path

Datapath I/O

- ° A wire can be driven by only one tri-state at a time
 - If InPass is active, AluPass must be inactive
 - If AluPass is active, InPass must be inactive



Datapath I/O

[°] Two values enter from the left (A and B)

- Need to perform (A+B)+A
- In -> X (Load A)
- In -> Y (Load B)
- A+B -> Y
- (A+B)+A -> Out

Four steps and then repeat



Implementing the Control ROM

0 Two values enter from the left (A and B)

- Need to perform (A+B)+A •
- In -> X (Load A) State 00 •
- In -> Y (Load B) State 01 ٠
- A+B -> Y State 10
- (A+B)+A -> Out State 11 •

NS

01

10

11

00

000

000

011

011

1

0

0

0

PS

00

01

10

11



More Complicated Example

- [°] Can we compute (A+B) . (A-B)?
- ° Currently, no place for intermediate storage
- ° Solution: Add RAM to datapath.



More Complicated Example

- ° Can we compute (A+B) . (A-B)?
 - Need to add intermediate storage.



Implementing the Control ROM

[°] Two values enter from the left (A and B)

- Need to perform (A+B). (A-B)
- In -> X (Load A) State 000
- In -> Y (Load B) State 001
- A+B -> RAM[4] State 010
- A-B -> X State 011
- RAM[4] ->Y State 100
- (A+B). (A-B) ->Out State 101

PS	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
000	001	000	1	0	1	0	0	000	0	0
001	010	000	0	1	1	0	0	000	0	0
010	011	011	0	0	0	1	0	100	0	1
011	100	010	1	0	0	1	0	000	0	0
100	101	000	0	1	0	0	0	100	1	0
101	000	110	0	0	0	1	1	000	0	0

Does the Value of the Data Matter?

- ° Problem: Add A to itself until overflow occurs
 - Amount of steps depends on A



Implementing the Control ROM using Conditions

One value enters from the left

0

Add A to itself until overflow occurs

- In -> X, Y (Load A, B) State 0 Next state 1
- X+Y -> Out, X State 1 Next state (1 if no overflow, 0 if overflow)

Include overflow (OF) bit as a ROM input Note that it doubles the size of the ROM

PS	OF	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
0	0	1	000	1	1	1	0	0	000	0	0
0	1	1	000	1	1	1	0	0	000	0	0
1	0	1	011	1	0	0	1	1	000	0	0
1	1	0	011	1	0	0	1	1	000	0	0

Bits in the ROM Each row indicates a ROM word

Implementing the Control ROM with Conditionals



- Overflow, carry out, zero
- Used to perform conditional operations

ı

 If statements and loops in programming languages



PS	OF	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
0	0	1	000	1	1	1	0	0	000	0	0
0	1	1	000	1	1	1	0	0	000	0	0
1	0	1	011	1	0	0	1	1	000	0	0
1	1	0	011	1	0	0	1	1	000	0	0

One More Example

- Read two values from RAM (locations 0 and 1) and store to location 2.
 - Very common operation for microprocessor



Implementing the Control ROM

- ° Perform memory reads and writes
 - RAM[0] -> X State 00
 - RAM[1] -> Y State 01
 - X+Y -> RAM[2] State 10

No interaction with outside interfaces (In, Out) is required

Very similar to microprocessor operations

PS	NS	Function	LoadX	LoadY	InPass	AluPass	OutPass	Addr	Read	Write
00 01	01 10	000 000	1 0	0 1	0 0	0 0	0 0	000 001	1 1	0 0
10	00	011	0	0	0	1	0	010	0	1

This slide marks the end of required material for this lecture!

Processor Construction Kit



Processor Compilation

- ° Software engineer writes C program
- ° Compiler software converts C to assembly code
- ° Assembler converts assembly code to binary format



A, B, and C are storage locations in main memory (DRAM)



Summary

- Datapaths are important components of computer systems
- ^o Interaction between control and data path determines <u>execution time</u>
- Each sequence of operations can be represented with a ROM program
 - Each row in the state table corresponds to a word in the ROM
- ^o Multiple rows for each state if the ROM has a control input (e.g. ALU overflow)
- ^o Next time: Notation to represent the data and control paths